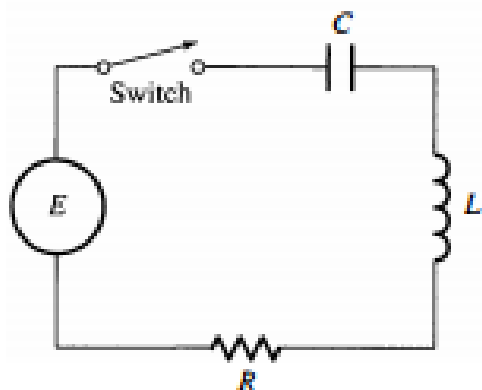


3.7: Electrical Circuits



| Circuit Element | Voltage Drop |
|-----------------|-------------------|
| Inductor | $L \frac{dI}{dt}$ |
| Resistor | RI |
| Capacitor | $\frac{1}{C} Q$ |

Here we examine an RLC electric circuit which consists of

1. A **resistor** with a resistance of R ohms.
2. An **inductor** with an inductance of L henries, and
3. A **capacitor** with a capacitance of C farads.

These objects are in a series after the electromotive force (such as a battery of generator) that supplies a voltage of $E(t)$ volts at time t . If the switch is closed, this results in a current of $I(t)$ amperes in the circuit and a charge of $Q(t)$ coulombs on the capacitor at time t . The relation between Q and I is given by

$$\frac{dQ}{dt} = I(t). \quad (1)$$

According to elementary properties of electricity, the **voltage drops** across the three circuit elements are shown above. With the help of Kirchoff's Law we arrive at the differential equation

$$L \frac{dI}{dt} + RI + \frac{1}{C} Q = E(t). \quad (2)$$

Substituting (2) into (1) we get the equation

$$LQ'' + RQ' + \frac{1}{C} Q = E(t) \quad (3)$$

for the charge Q , or more commonly,

$$LI'' + RI' + \frac{1}{C} I = E'(t) \quad (4)$$

for the current I .

Question 1. Does this look familiar to the mass-spring-dashpot mechanical system

$$mx'' + cx' + kx = F(t)$$

from Section 3.4 and 3.6? What transformations would you make to create a **mechanical-electrical analogy**?

Question 2. Why would this analogy be useful in practice?

Example 1. Consider an RLC circuit with $R = 50$ ohms (Ω), $L = 0.1$ henry (H), and $C = 5 \times 10^{-4}$ farad (F). At time $t = 0$, when both $I(0)$ and $E(0)$ are zero, the circuit is connected to a 110-V, 60-Hz alternating current generator. Find the current in the circuit and the time lag of the steady periodic current behind the voltage.

Homework. 1, 7, 11-15 (odd)